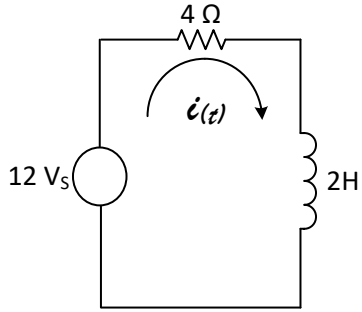


1. A 12 V battery is connected at $t = 0$.

$$R = 4\Omega$$

$$L = 2\text{H}$$

Find $i(t)$.




2. Same circuit but **initial current = 2 A**.

$$R = 4\Omega$$

$$L = 2\text{H}$$

Find $i(t)$.

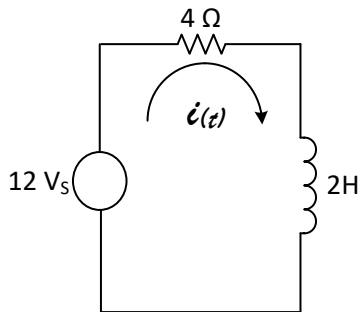


3. Battery removed at $t = 0$.

Initial current $5A$

$R = 5\Omega$

$L = 1H$

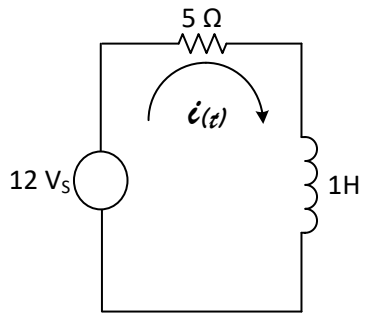


4. Voltage source

$v(t) = 10u(t)$

$R = 2\Omega$

$L = 1H$

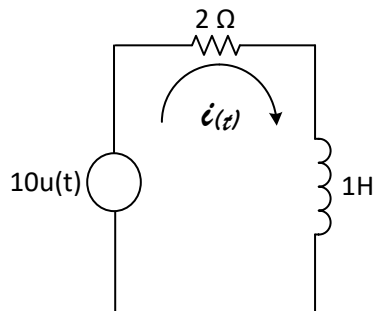


5. Step voltage

$$v(t) = 20u(t)$$

$$R = 10\Omega$$

$$L = 2\text{H}$$

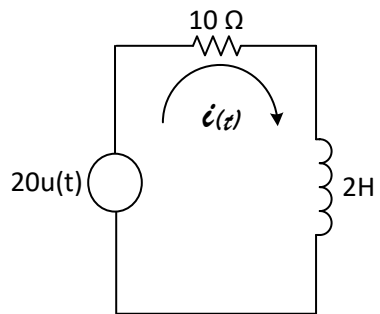


6. Impulse input

$$5v(t) = 5\delta(t)$$

$$R = 1\Omega$$

$$L = 1\text{H}$$

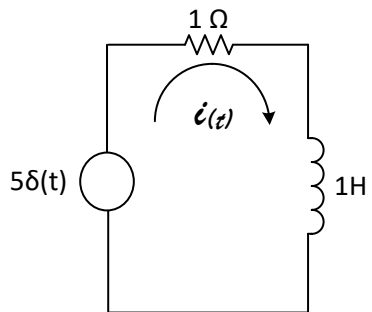


7. Ramp input

$$v(t) = 10t$$

$$R = 5\Omega$$

$$L = 1\text{H}$$

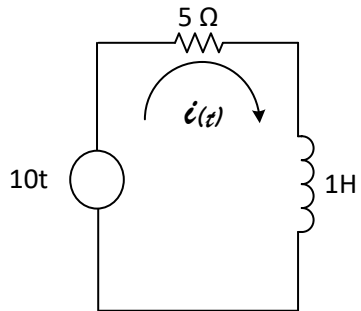


8. Initial current = 3A

$$V = 9\text{V}$$

$$R = 3\Omega$$


$$L = 1\text{H}$$

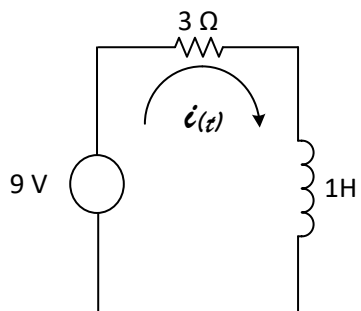

9. 10V step

$$R = 5\Omega$$

$$C = 0.2F$$

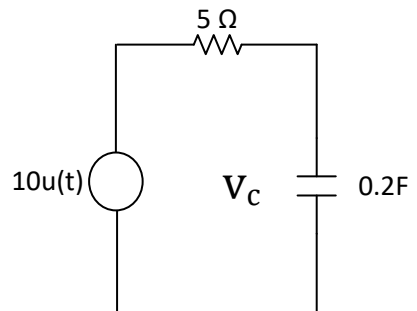


10. Initial capacitor voltage 4V

20V source

$$R = 10\Omega$$

$$C = 0.5F$$

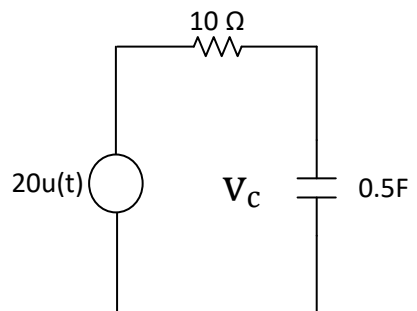


11. Discharge

Initial 10V

$R = 5\Omega$

$C = 0.5F$

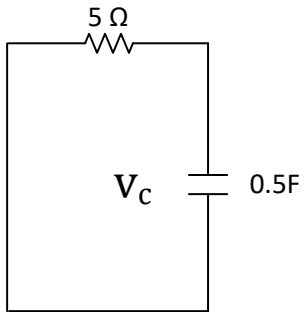


12. Input

$v(t) = 15u(t)$

$R = 3\Omega$

$C = 1F$

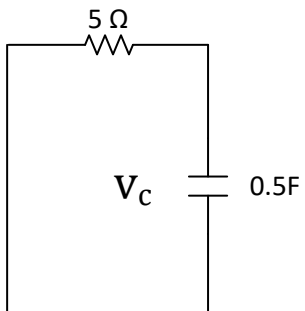


13. Impulse input

$$v(t) = 5\delta(t)$$

$$R = 1\Omega$$

$$C = 1F$$

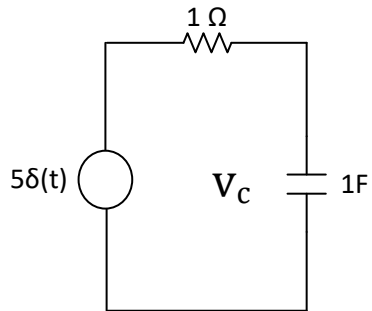


14. Ramp input

$$v(t) = 10t$$


$$R = 2\Omega$$

$$C = 0.5F$$

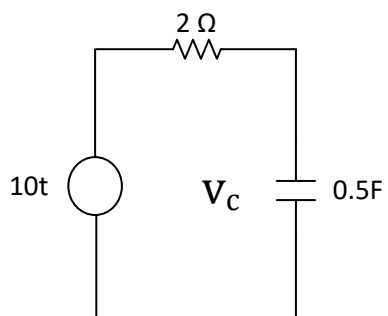


15. Sinusoidal forcing

$$v(t) = 10\sin(2t)$$

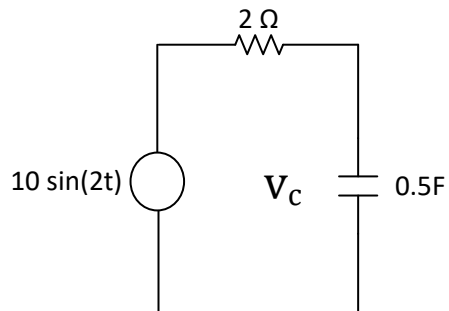

16. Initial voltage across capacitor = +6V

Source = 12V

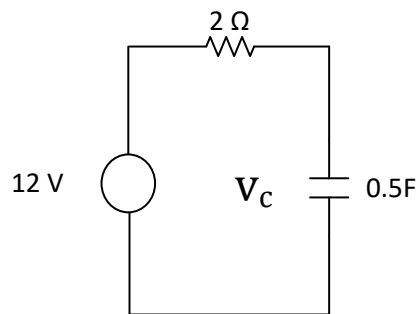


17. Series RLC

$$R = 4\Omega$$

$$L = 1\text{H}$$

$$C = 0.25\text{F}$$

$$V = 12\text{V}$$

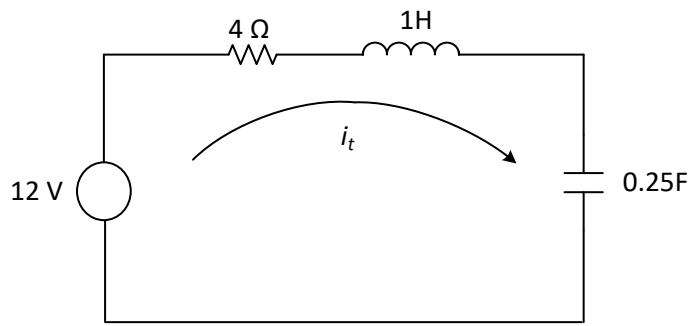


18. Underdamped case

$$R = 2\Omega$$

$$L = 1\text{H}$$

$$C = 1\text{F}$$

$$V = 10\text{V}$$

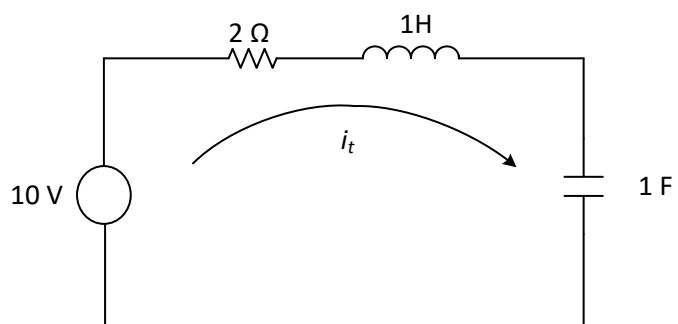


19. Underdamped again

$$R = 3\Omega$$

$$L = 1\text{H}$$

$$C = 1\text{F}$$

$$V = 12\text{V}$$

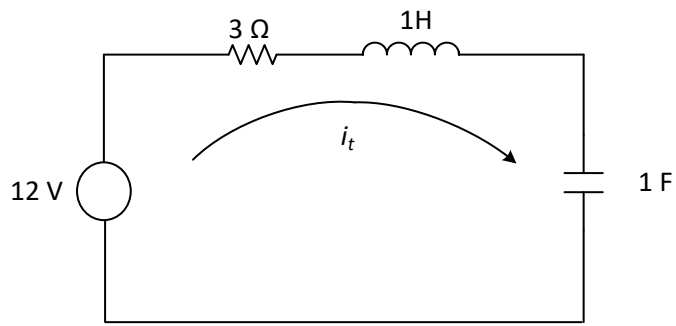


20. Critical damping

$$R = 4\Omega$$

$$L = 1\text{H}$$

$$C = 0.25\text{F}$$

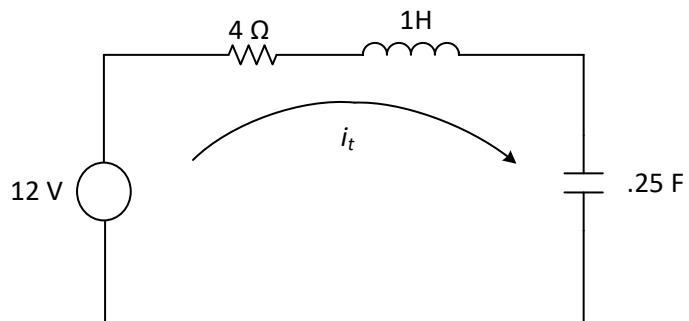


21. Overdamped

$$R = 6\Omega$$


$$L = 1\text{H}$$

$$C = 1\text{F}$$

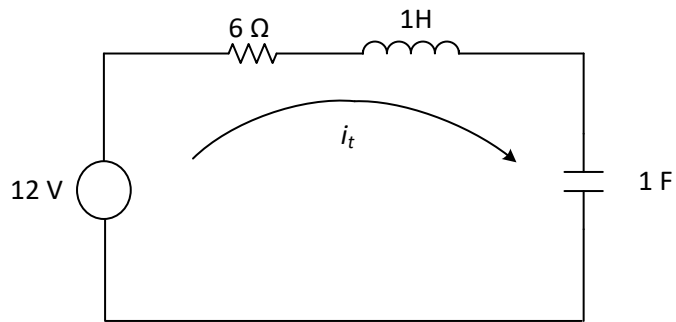


22. Sinusoidal forcing

$$v(t) = 10\sin(3t)$$

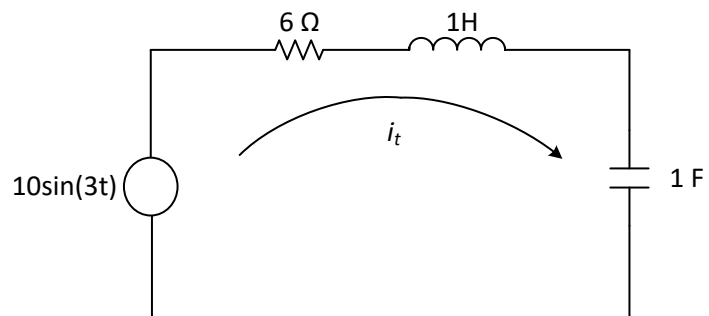

23. Impulse input

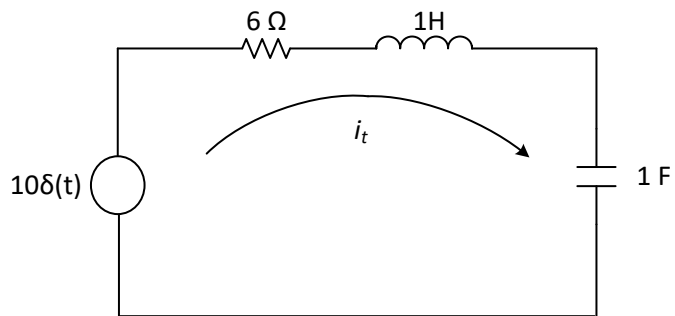

24. Current source applied at $t = 0$

$$i_s(t) = 6u(t)A$$

$$R = 3 \Omega$$


$$L = 1 H$$

$$C = 0.5 F$$

Initial conditions

$$v(0) = 0, i_L(0) = 0$$

Find $v(t)$.

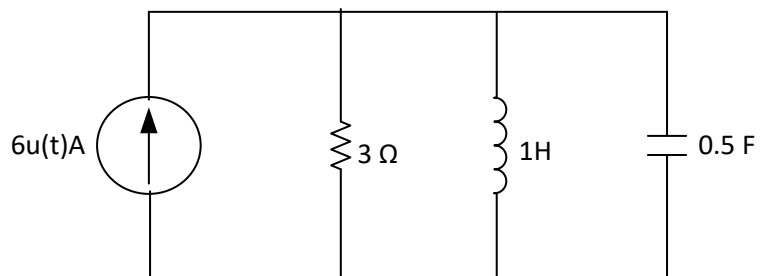

25. Voltage source applied


$$v_s(t) = 12u(t)$$

$$R = 6 \Omega$$

$$L = 2 \text{ H}$$

$$C = 0.5 \text{ F}$$

Find inductor current $i_L(t)$.

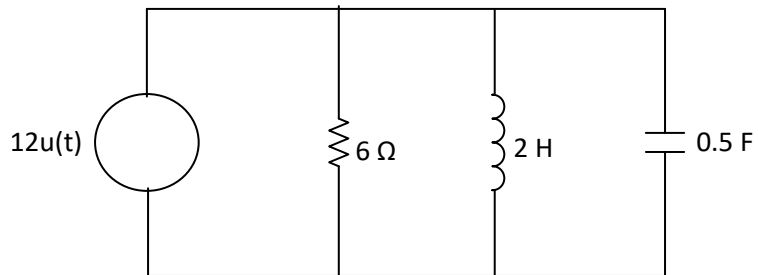

26. Current source

$$i_s(t) = 10u(t)$$

$$R = 5 \Omega$$


$$L = 1 \text{ H}$$

$$C = 1 \text{ F}$$

Initial conditions

$$v(0) = 0$$

Find $v(t)$.

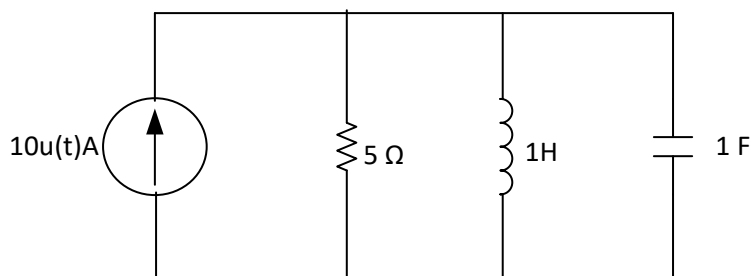

27. Impulse current source


$$i_s(t) = 5\delta(t)$$

$$R = 2 \Omega$$

$$L = 1 \text{ H}$$

$$C = 1 \text{ F}$$

Find $v(t)$

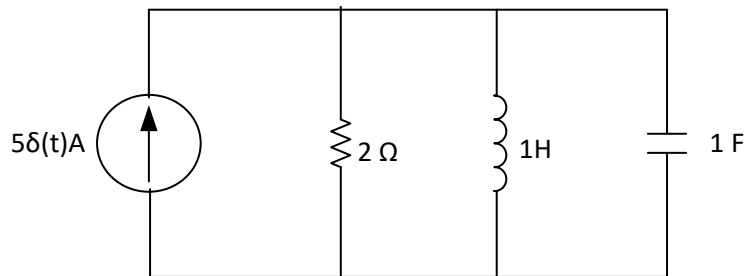

28. Sinusoidal current source


$$i_s(t) = 8\sin(2t)$$

$$R = 4 \Omega$$

$$L = 1 \text{ H}$$

$$C = 0.25 \text{ F}$$

Find steady-state voltage.

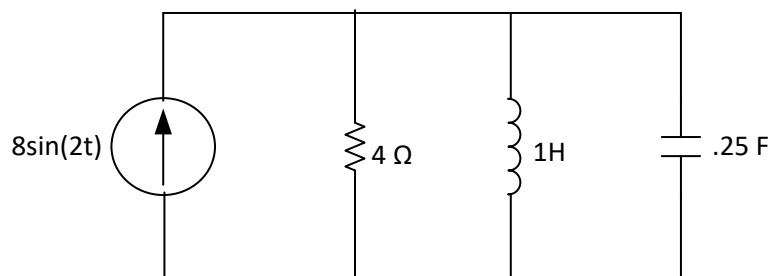

29. Step current source

$$i_s(t) = 6u(t)$$

$$R = 6 \Omega$$


$$L = 1 \text{ H}$$

$$C = 0.5 \text{ F}$$

Initial voltage

$$v(0) = 4V$$

Find $v(t)$

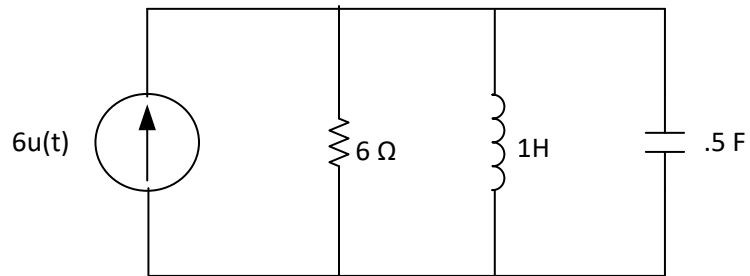

30. Ramp current source


$$i_s(t) = 4t$$

$$R = 2 \Omega$$

$$L = 1 \text{ H}$$

$$C = 0.5 \text{ F}$$

Find $v(t)$

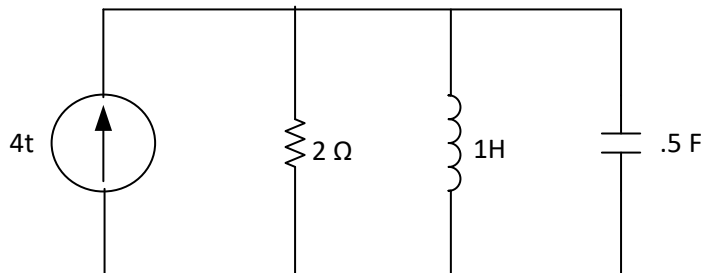

31: Parallel RLC with initial conditions

$$R = 3 \Omega$$

$$L = 1 \text{ H}$$


$$C = 1 \text{ F}$$

Initial

$$v(0) = 6V, i_L(0) = 0$$

No source (natural response)

Find $v(t)$

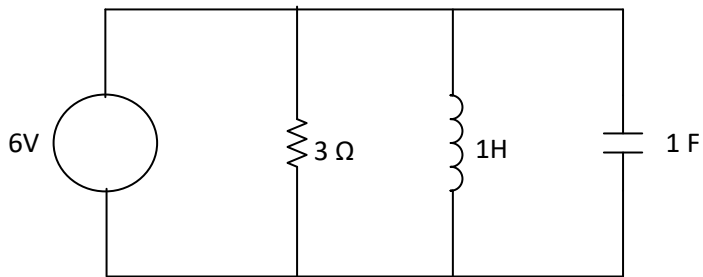

32. Current source


$$i_s(t) = 10u(t)$$

$$R = 5 \Omega$$

$$L = 2 \text{ H}$$

$$C = 0.25 \text{ F}$$

Find $v(t)$

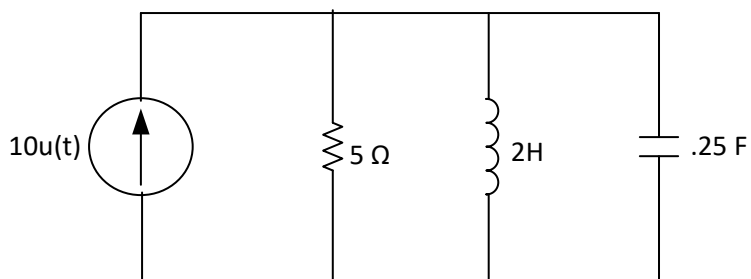

33. Sinusoidal current source


$$i_s(t) = 12\sin(3t)$$

$$R = 6 \Omega$$

$$L = 2 \text{ H}$$

$$C = 0.5 \text{ F}$$

Find steady-state voltage.

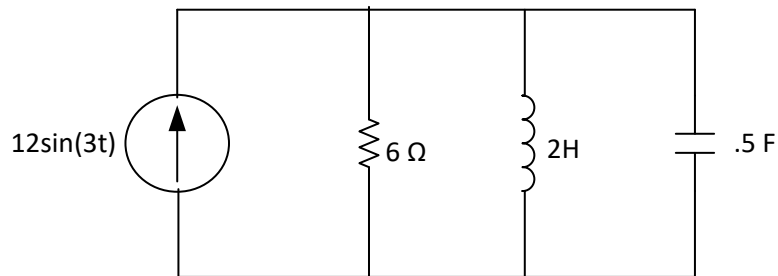


34. Find $v_o(t)$ across the capacitor.

$$R_1 = 4 \Omega$$

$$R_2 = 6 \Omega$$

$$C = 0.5 \text{ F}$$


Initial capacitor voltage = 0

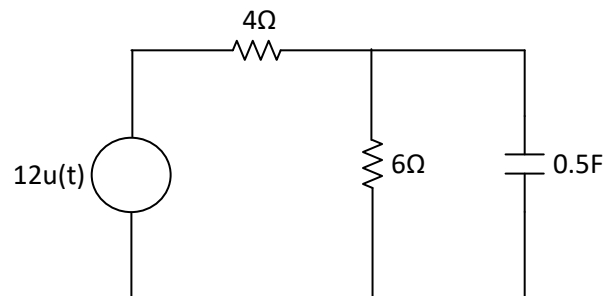

35. Series RL Feeding Parallel RC

Find $v_o(t)$ across the capacitor.

Initial conditions = 0.

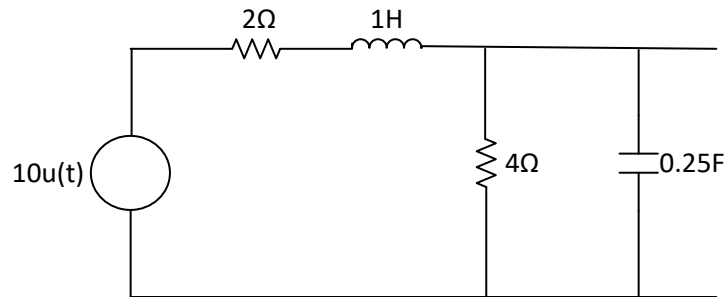

36. Series RLC Feeding Parallel R

Find $v_o(t)$ across the parallel resistor.

$15u(t)$


$R_1=3\Omega$

$L=1H$

$C=0.5F$

$R_2=6\Omega$

Initial conditions = 0

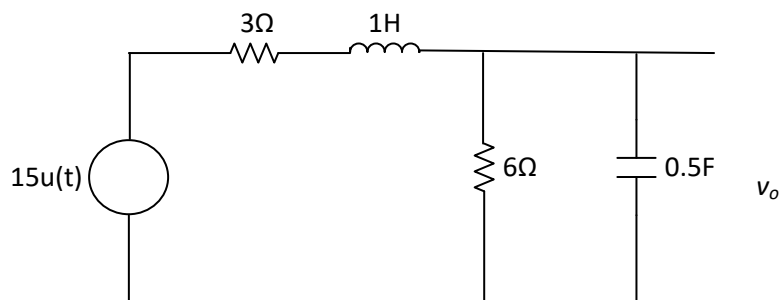


37. Parallel RC After Series Divider

Find $v_o(t)$.

$20u(t)$

$R_1=5\Omega$

Initial capacitor voltage = 5 V.

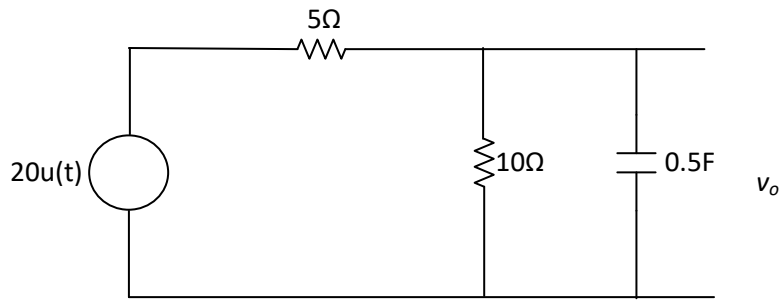

38. Series R Feeding Parallel RLC

Find $v_o(t)$

$24u(t)$

$R_1=4\Omega$


$R_2=6\Omega$

$L=1H$

$C=0.25F$

$v_o(t)$

Initial conditions = 0

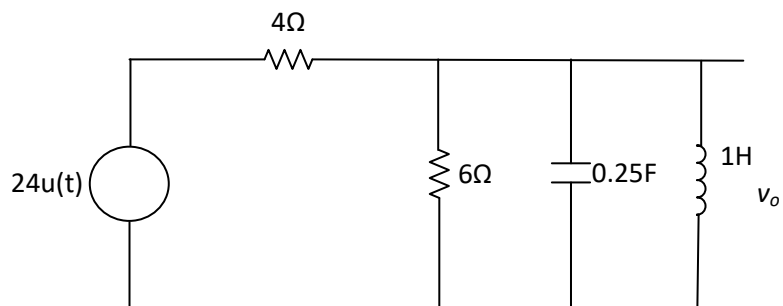

39. Series RL feeding parallel RC (2nd order)

$$20u(t)$$

$$R_1=4\Omega$$

$$L=1H$$


$$R_2=6\Omega$$

$$C=0.25F$$

$$v_o(t)$$

Initial conditions: zero

Find $v_o(t)$.

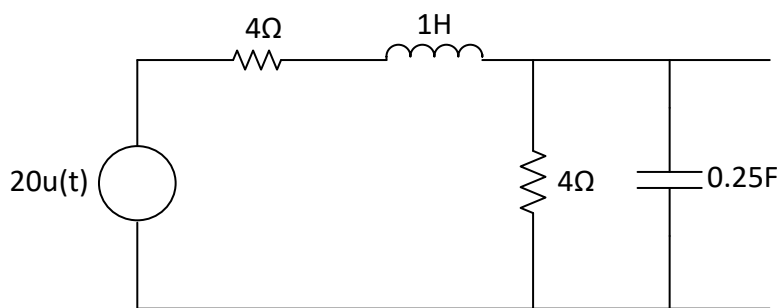

40. Series RLC feeding load resistor

$$15u(t)$$


$$R_1=3\Omega$$

$$L=1H$$

$$C=0.5$$


$$R_2=6\Omega$$

Find $v_o(t)$.

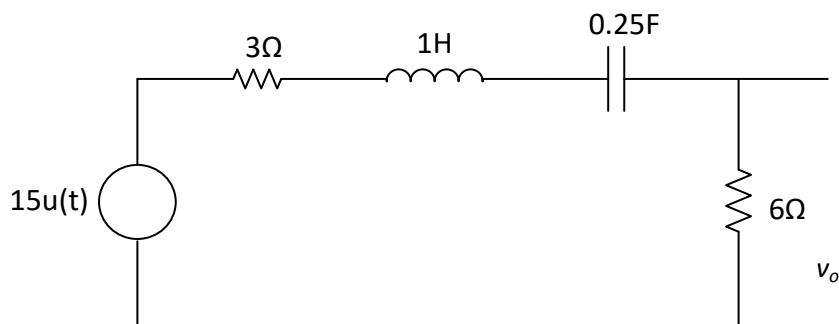

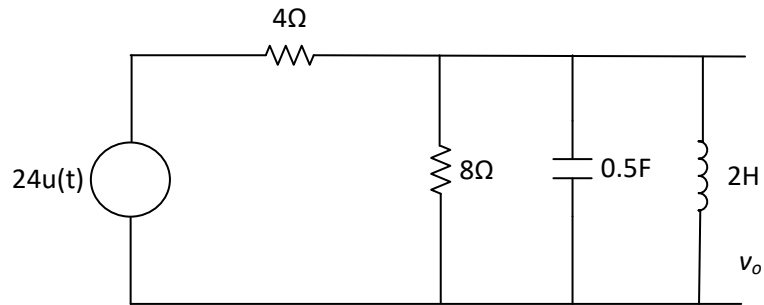
41. Series R feeding parallel RLC

$24u(t)$
 $R_1=4\Omega$
 $R_2=8\Omega$
 $L=2H$
 $C=0.5F$
Find $v_o(t)$.



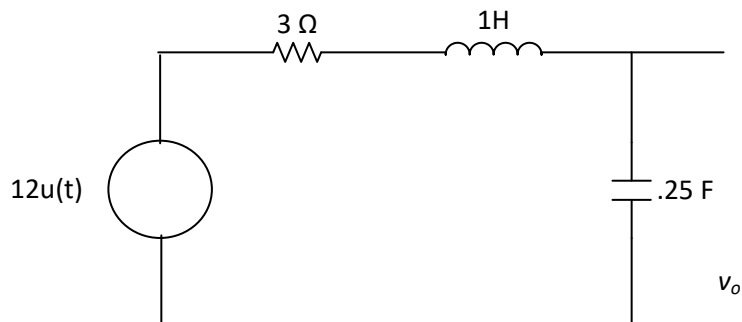42. Series RL with capacitor output

Find capacitor voltage $v_o(t)$.
 $12u(t)$
 $R=3\Omega$
 $L=1H$
 $C=0.25F$



43. Parallel RLC fed through series resistor

Find $v_o(t)$.


$18u(t)$

$R_1=2\Omega$

$R_2=6\Omega$

$L=1H$

$C=0.5F$

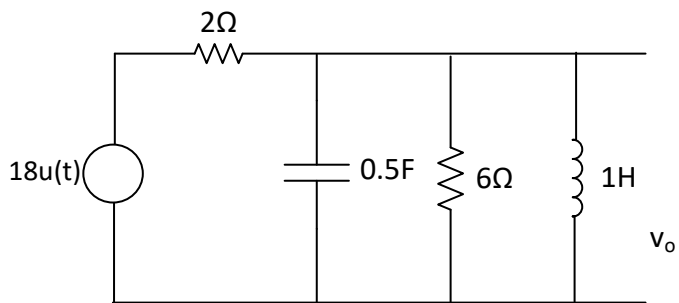

44. Series RLC with capacitor output


Find $v_o(t)$.

$10u(t)$

$R=2\Omega$

$L=1H$

$C=0.5F$

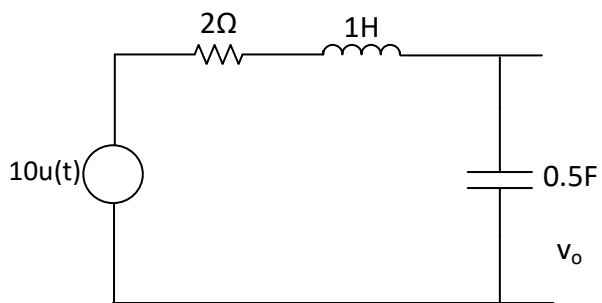

45. Parallel RC branch after RL

Find $v_o(t)$.


$16u(t)$

$R_1=4\Omega$

$L=2H$

$R_2=8\Omega$

$C=0.25F$

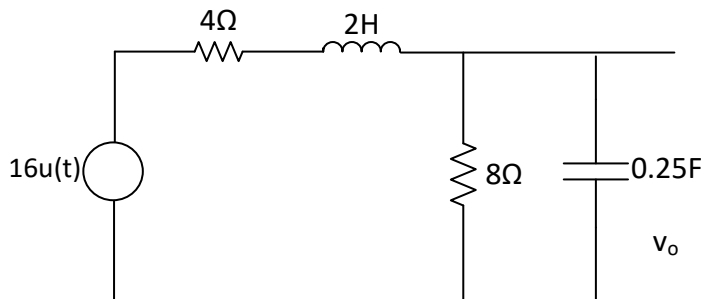

46. Harder mixed RLC network

Find $v_o(t)$.


$30u(t)$

$R_1=6\Omega$

$L=2H$


$R_2=12\Omega$

$C=0.5F$

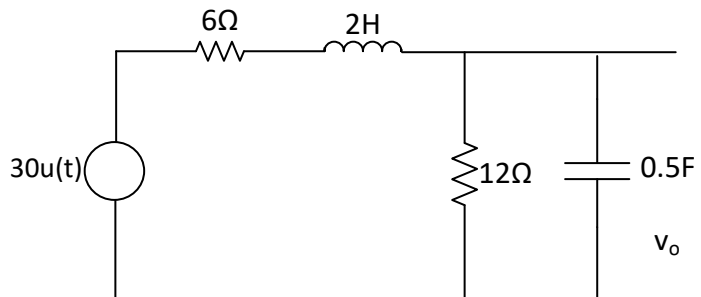

47. Two Mesh RL-RC Circuit

Find the mesh currents.

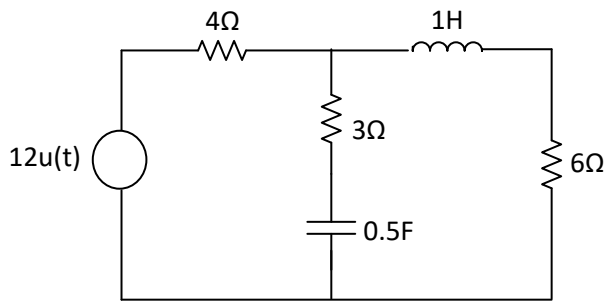


Let Initial conditions = 0.

$i_1(t)$ = left mesh

$i_2(t)$ = right mesh

48. Two Mesh RLC Circuit (Second Order)

Find $i_1(t)$ and $i_2(t)$.

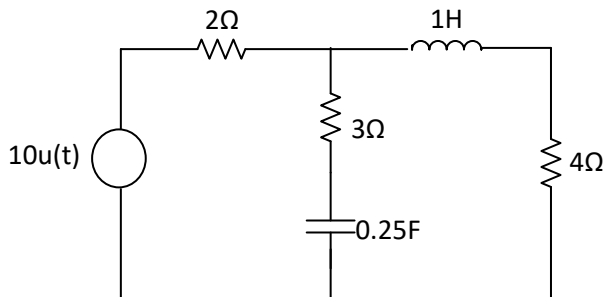


Initial conditions


$i_L(0) = 2A$

$v_C(0) = 4V$


49. Find i_1 and i_2 in the following:

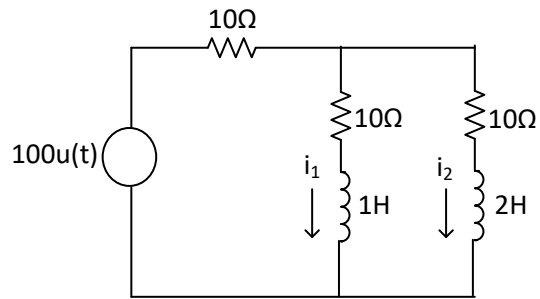

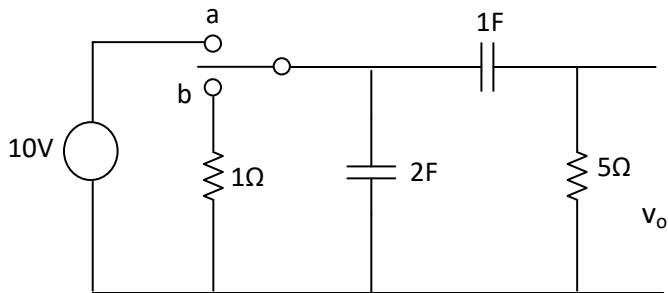
50. The switch changes from a to b at $t = 0$. Write the equation for v_o .



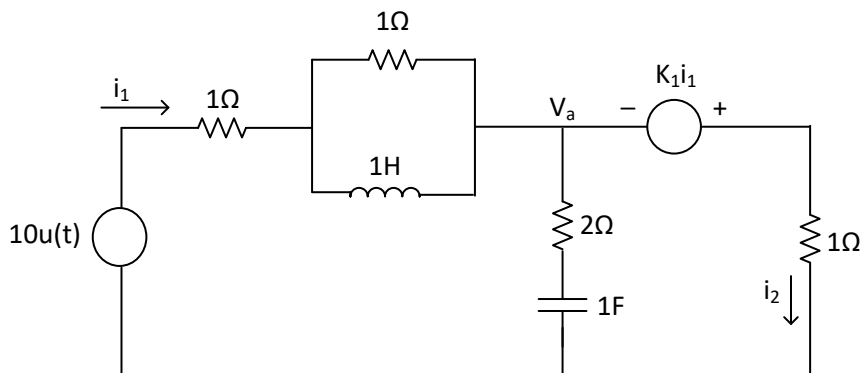
51. For the following, determine V_a with $K_1 = -3$




52. Find V_o :

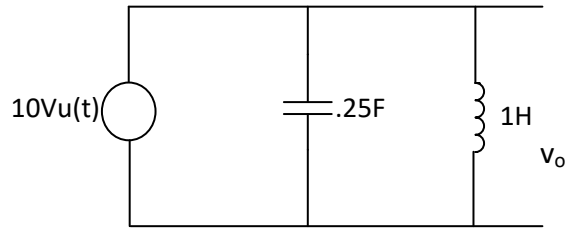

53. Find V_o :

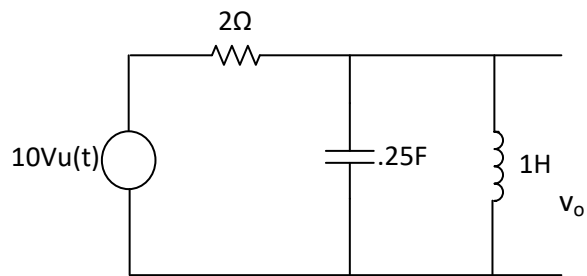

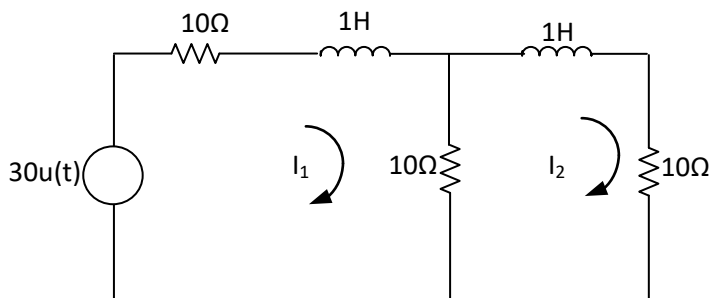54. Find the current I_2 in the following:



55. Find the voltage across the 5Ω Resistor at right:

